

An optimised 4-bit carry look ahead adder to minimize delay

Kaamya Dasika

2023102034

UG2, ECE

IIIT Hyderabad

Abstract— In this paper, an optimized 4-bit carry look-ahead adder (CLA) design is proposed to minimize propagation delay in digital circuits. The conventional ripple carry adder is transformed to utilize two-level carry logic, significantly reducing delay while maintaining accurate output at the next clock edge. Key optimizations include the use of CMOS static logic gates, transistor sizing for balanced rise and fall times, and the adoption of edge-triggered flip-flops to align with the timing diagram. The design prioritizes speed by assuming stable inputs within specific timing constraints, offering a trade-off between performance and input variability tolerance. Simulation results from NGSPICE demonstrate reduced delays and improved clock speed, validated through pre-layout and post-layout analyses. Implementation on FPGA further verifies the design's performance, showcasing efficient addition with high-speed operation.

Keywords: Carry Look-Ahead Adder, CMOS Logic, Delay Optimization, FPGA, NGSPICE, Digital Design

I. INTRODUCTION

A carry look-ahead adder reduces the propagation delay by introducing more complex hardware. In this design, the ripple carry design is suitably transformed such that the carry logic over fixed groups of bits of the adder is reduced to two-level logic. We shall design a CLA considering that input bits are available before the rising edge of the clock and the output should be computed and present at the next rising edge of the clock. We achieve this using D flip flops and the input and output. To reduce the delay, we optimize the propagate and generate terms.

II. CONVENTIONAL STRUCTURE

By generating carry signals quickly, the CLA enhances the speed of binary addition.

A. Inputs and Outputs

Inputs: Two 4-bit binary numbers $A=(A_3,A_2,A_1,A_0)$ and $B=(B_3,B_2,B_1,B_0)$, along with an initial carry-in C_{in} .
Outputs: A 4-bit sum $S=(S_3,S_2,S_1,S_0)$ and a final carry-out C_{out} .

B. Generate and Propagate terms

- For each bit position i , Generate and Propagate signals are derived as:
 $G_i = A_i \text{ XOR } B_i$ $P_i = A_i + B_i$

These signals are used to calculate carry signals independently of previous bits, allowing carry information to be determined concurrently.

C. Carry Lookahead Logic

- Carry-out signals are generated for each bit position in advance:

$$C_1 = G_0 + (P_0 \cdot C_{in})$$

$$C_2 = G_1 + (P_1 \cdot C_1) = G_1 + (P_1 \cdot (G_0 + P_0 \cdot C_{in}))$$


$$C_3 = G_2 + (P_2 \cdot C_2)$$

$$C_{out} = G_3 + (P_3 \cdot C_3)$$

Using the carry signals, each bit of the sum S_i is computed as: $S_i = P_i \oplus C_i$

- This parallelized calculation of carry signals reduces the delay associated with traditional ripple-carry adders.

III. PROPOSED STRUCTURE

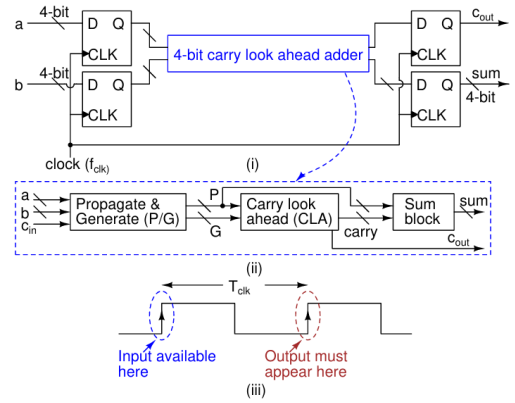

The proposed structure has OR logic for finding P_i terms.

Since the result of XOR and OR differ in the cases when both A and B are 1, and in this case the C_{i+1} is independent of C_i and P_i , we don't have to worry about any mismatch. This reduces the complexity of the design. Since complementary logic gates are inverting in CMOS static logic, it is more efficient to deal with NAND and NOR (universal gates) in CMOS rather than AND and OR. So we do the following changes using DeMorgan's theorem-

$$P'_i = \overline{A_i + B_i}$$

$$G'_i = \overline{A_i \cdot B_i}$$

$$C_1 = \overline{G'_0 \cdot (P'_0 + \overline{C_0})}$$

$$C_2 = \overline{G'_1 \cdot (P'_1 + G'_0) + (\overline{P'_1 + P'_0} \cdot C_0)}$$


$$C_3 = \overline{G'_2 \cdot (P'_2 + G'_1) + (\overline{P'_2 + P'_1} \cdot \overline{G'_0(P'_0 + \overline{C_0})})}$$

$$C_4 = \overline{P'_3 + P'_2 \cdot \overline{P'_1 + P'_0} \cdot C_0 + G'_3 \cdot (P'_3 + G'_2) + (\overline{P'_3 + P'_2} \cdot \overline{G'_1(P'_1 + G'_0)})}$$

CI	AI	BI	AI XOR Bi	AI OR Bi	AI AND Bi	CI+1	Carry type
0	0	0	0	0	0	0	None
0	0	1	1	1	0	0	None
0	1	0	1	1	0	0	None
0	1	1	0	1	1	1	Generate
1	0	0	0	0	0	0	None
1	0	1	1	1	0	1	Propagate
1	1	0	1	1	0	1	Propagate
1	1	1	0	1	1	1	Generate/Propagate



In this design, a negative edge flipflop has been used at the input side and a positive edge flip flop at the output side to get the results according to the timing diagram. So since inputs are available at the +ve edge itself, we consider them at the immediate -ve edge. Although any changes in the input in this time span between a consecutive +ve and -ve edge will affect the output, but the design has been made with an assumption that no change occurs. This decreases the delay of the circuit as we give outputs immediately at the upcoming +ve edge. This is the trade off of the implementation- more speed/ less delay with the input not changing till the -ve edge after they have been provided.

A. Circuit Diagram

 

 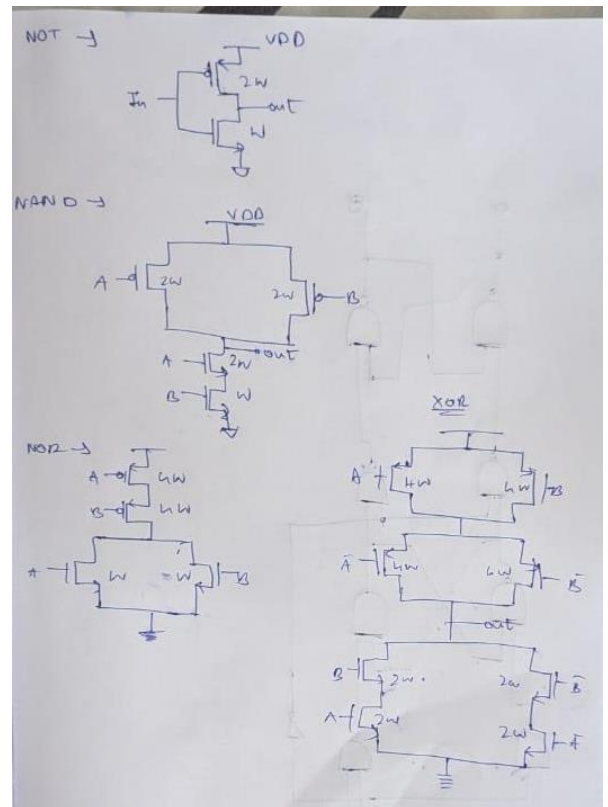IV. DESIGN DETAILS


- The width of the transistors in each of the gates have been decided to match that of the ideal inverter in order to obtain equal rise and fall times and minimize delays and uncertainties. The drive a 20 LAMBDA/10 LAMBDA inverter.
- CMOS static logic is being used for all gates in the circuit, the sizes are as follows-




V. NGSPICE SIMULATIONS



```
.tran in 600n
.measure tran tpd1
+TRIG v(y1) VAL='0.50*SUPPLY' RISE=1 TARG v(p1) VAL='0.50*SUPPLY' RISE=1
.measure tran tpdf1
+TRIG v(y1) VAL='0.50*SUPPLY' FALL=1 TARG v(p1) VAL='0.50*SUPPLY' FALL=1
.measure tran tpd1
+param=(tpd1+tpdf1)/2' goal=0
```

A. Adder block-

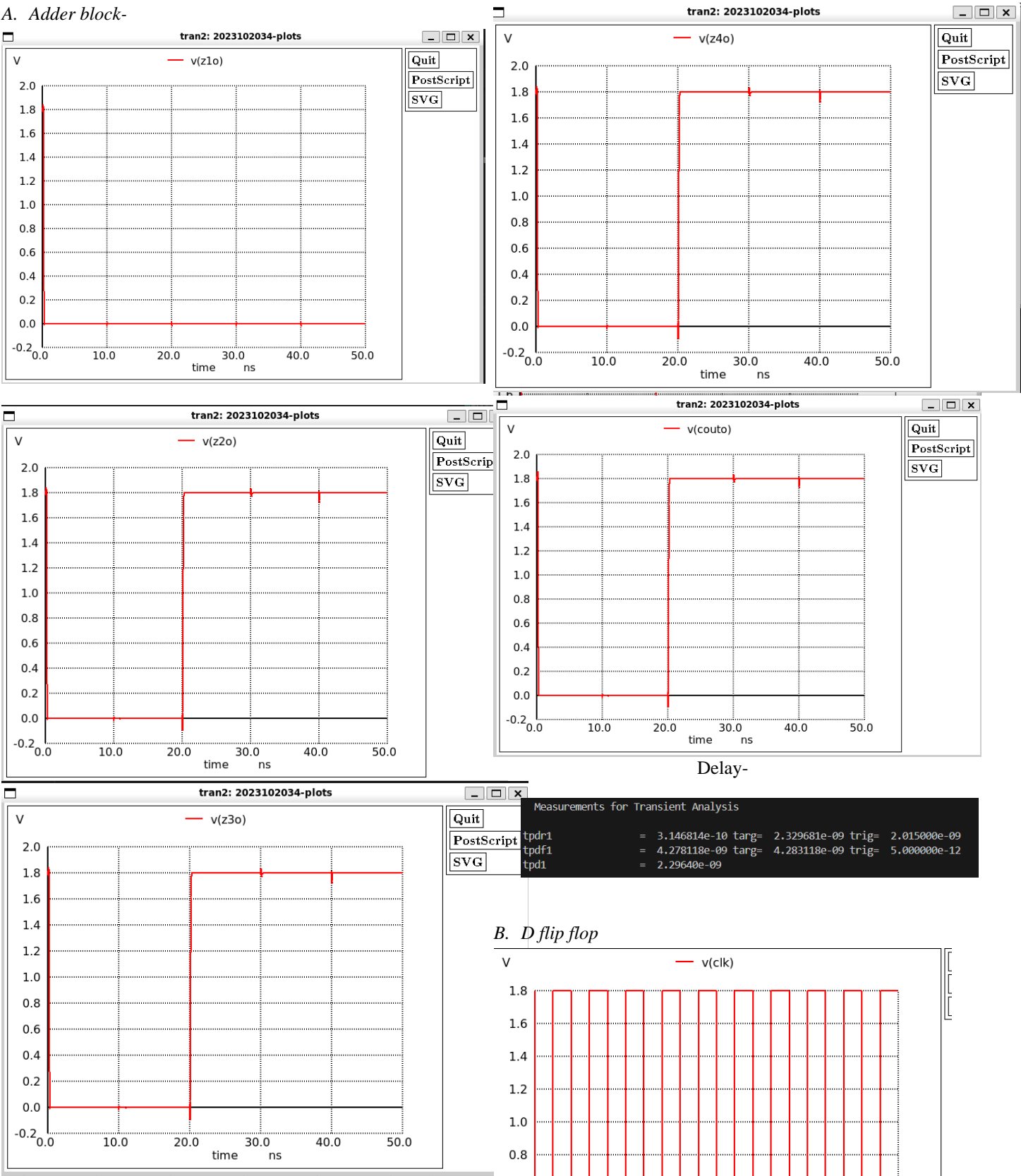


B. D flip flop

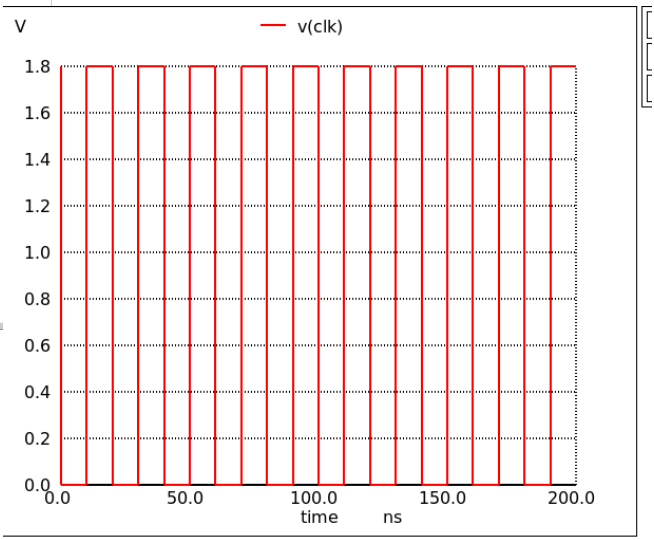

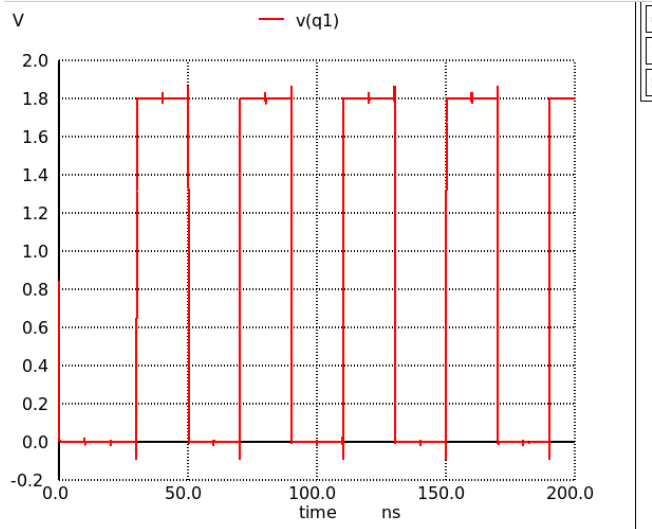 

C. P, G terms-

 

```
Measurements for Transient Analysis
tpdr1      = -1.968730e-09 targ= 4.626997e-11 trig= 2.015000e-09
tpdf1      = 2.039457e-09 targ= 2.044457e-09 trig= 5.000000e-12
tpd1       = 3.53633e-11
```

VI. D FLIP FLOP DELAYS

A. Setup time-

```
No. of Data Rows : 238
Measurements for Transient Analysis
setup_time    = 2.500000e-10 targ= 6.500000e-09 trig= 6.250000e-09
ngspice 22 -> []
```

B. Hold time-


```
No. of Data Rows : 238
Measurements for Transient Analysis
hold_time     = 0.000000e+00 targ= 6.500000e-09 trig= 6.500000e-09
ngspice 41 -> d1.cir
```

C. TPCQ delay(contamination delay)


```
ngspice 43
xiff.x9.1      0.0384786
vd#branch      0
vclk1#branch    0
vdd#branch     -1.23530e-10

No. of Data Rows : 238
Measurements for Transient Analysis
clkq_time     = 2.540509e-10 targ= 1.675405e-08 trig= 1.650000e-08
ngspice 1 ->
```


VII. STICK DIAGRAMS

 


A. NAND

 


B. NOR

 




C. XOR

 


D. INVERTER

 




VIII.FINAL CIRCUIT PRE LAYOUT

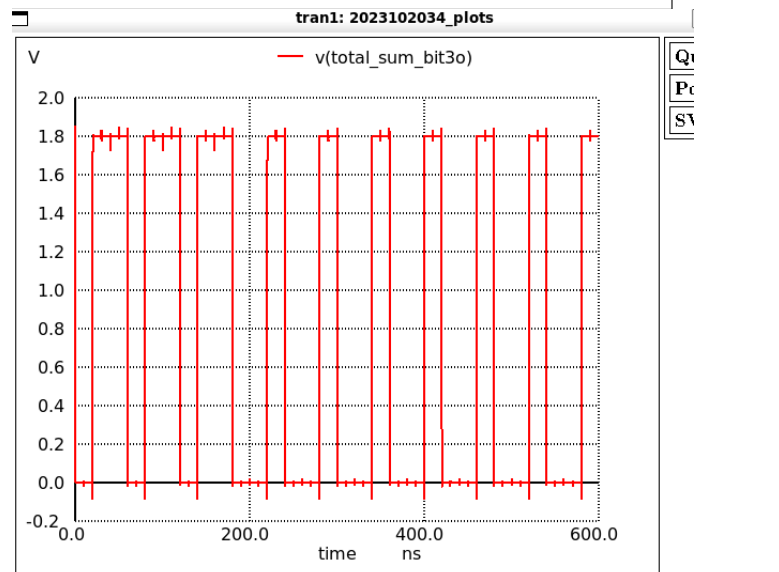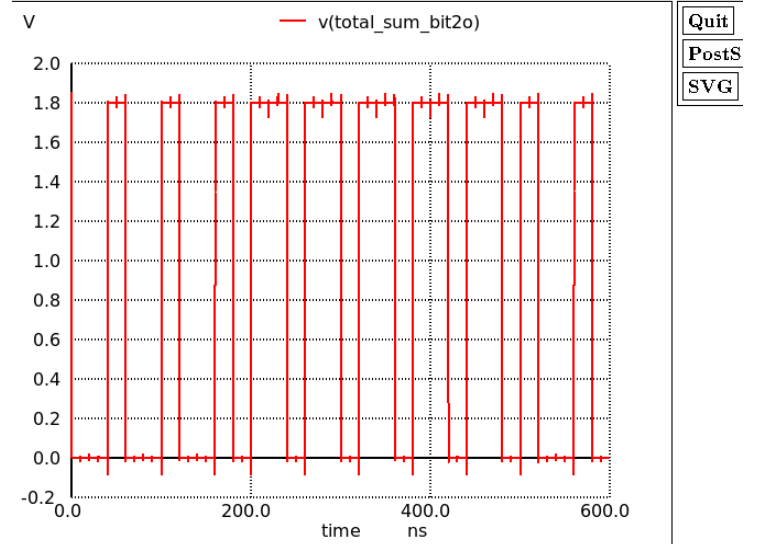 

IX. POSTLAYOUT

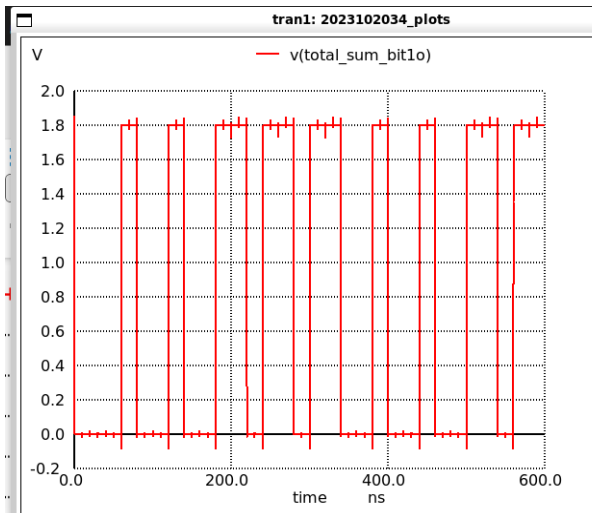

A. Adder block-

 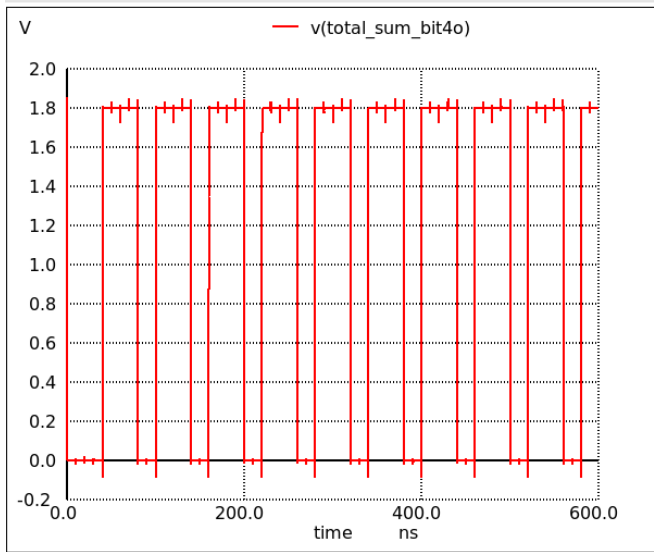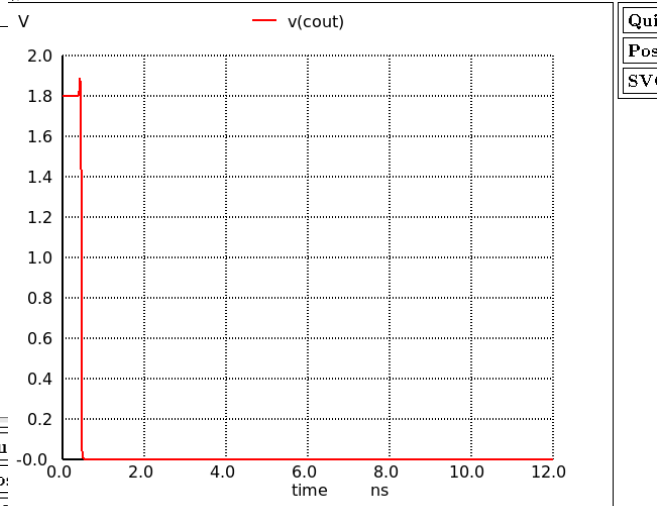

A. Delay of full circuit-

```
No. of Data Rows : 6973

Measurements for Transient Analysis

tpdr1      = 1.981090e-07 targ= 2.001240e-07 trig= 2.015000e-09
tpdf1      = 1.769200e-10 targ= 1.819200e-10 trig= 5.000000e-12
tpd1       = 9.91430e-08

,hardcopy: no such command available in ngspice
v(v15a) v15out offset= on each command available in ngspice
```

B. Worst case delay of adder-

```
tpdr1      = 3.146814e-10 targ= 2.329681e-09 trig= 2.015000e-09
tpdf1      = 4.278118e-09 targ= 4.283118e-09 trig= 5.000000e-12
tpd1       = 2.29640e-09
```

C. Maximum Clock speed-


$$T_{\text{clk min}} = 2.7 \text{ ns}$$


$$T_{\text{clk}} \geq t_{\text{PCQ max}} + t_{\text{PD max}} + t_{\text{setup}}$$

I can see that the value matches with this and there is no setup time violation as $t_{\text{PCQ max}} = 0.25 \text{ ns}$

$$t_{\text{PD max}} = 2.2 \text{ ns}$$

$$t_{\text{setup}} = 0.25 \text{ ns}$$

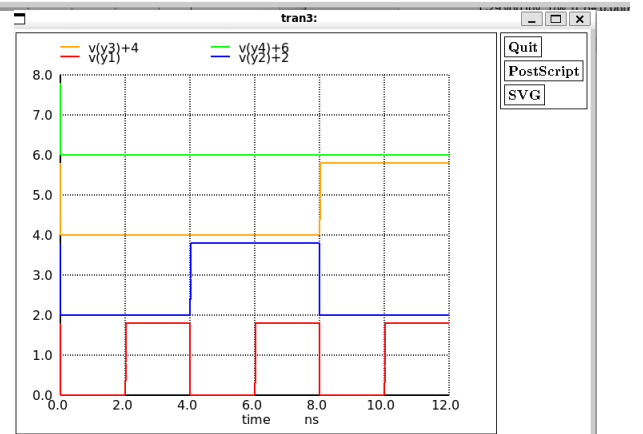

 


Delay-

```

tpdr1      = 2.814415e-10 targ= 2.296442e-09 trig= 2.015000e-09
tpdf1      = 4.253997e-09 targ= 4.258997e-09 trig= 5.000000e-12
tpd1       = 2.26772e-09

```

B. P, G block

 

Delay-


Measurements for Transient Analysis

```

tpdr1      = -1.964972e-09 targ= 5.002753e-11 trig= 2.015000e-09
tpdf1      = 2.043485e-09 targ= 2.048485e-09 trig= 5.000000e-12
tpd1       = 3.92561e-11



```



C. D flip flop

 

X. FINAL CIRCUIT POST LAYOUT

Simulations-

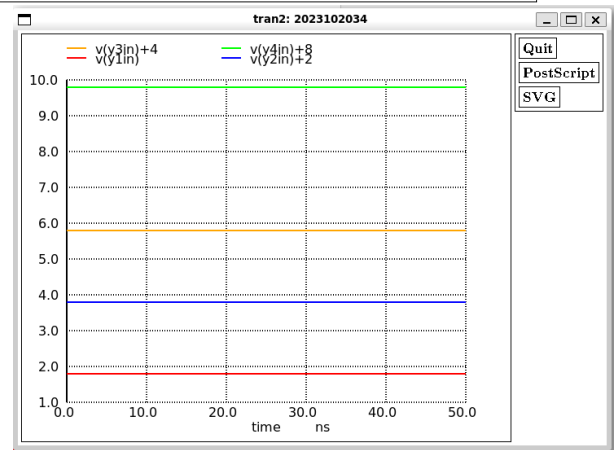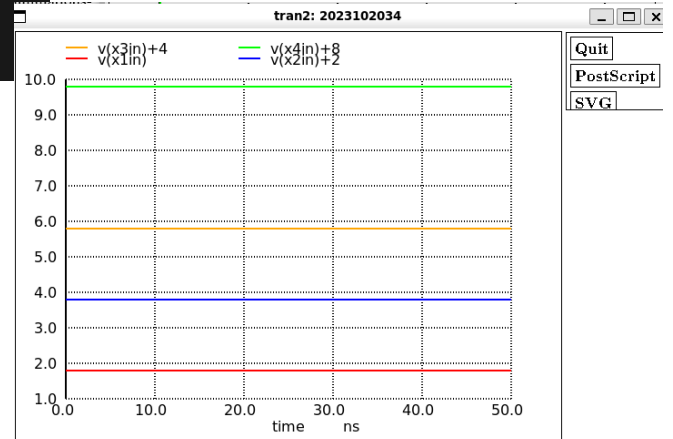

  

Delay-

```
Measurements for Transient Analysis
tpdr1      = 1.988999e-07 targ= 2.001149e-07 trig= 2.015000e-09
tpdf1      = 2.201641e-07 targ= 2.201691e-07 trig= 5.000000e-12
tpd1       = 2.09132e-07
.hardcopy: no such command available in ngspice
v(y1in)+4*input_offset: no such command available in ngspice
v(y4in)+7*input_offset: no such command available in ngspice
```

XI. D FLIP FLOP POST LAYOUT DELAY

Delay-

$$T_{clk} \geq t_{PCQ \max} + t_{PD \max} + t_{setup}$$

$$t_{PCQ \max} = 0.38 \text{ ns}$$

$$t_{PD \max} = 2.2 \text{ ns}$$

$$t_{setup} = 0.25 \text{ ns}$$

$$\text{thus } T_{clk \min} \text{ is } 2.83 \text{ ns}$$

A. Hold time-

```
Measurements for Transient Analysis
hold_time   = 2.000950e-21 targ= 6.500000e-09 trig= 6.500000e-09
ngspice 42 ->
```

B. Tpcq-

```
ngspice 42 ->
hand_1/a      0.701268
vd#branch     -1.65886e-07
vc1#branch    -1.34991e-07
vdd#branch    -0.000245982


No. of Data Rows : 238

Measurements for Transient Analysis
clkq_time     = 3.844780e-10 targ= 6.884478e-09 trig= 6.500000e-09
ngspice 1 ->
```


XII. MAGIC

A. Layouts-



Full circuit-

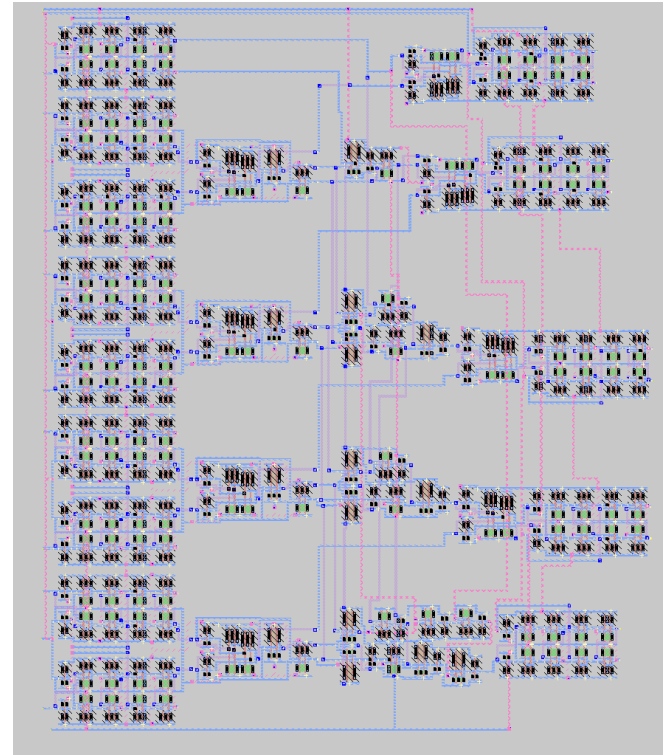


Adder-

 


Flip flop-

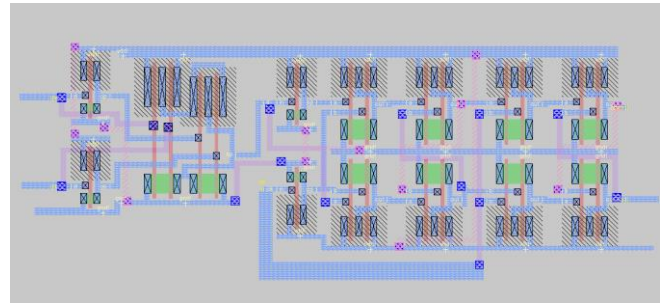 

P, G generation-

 


Inverter-

 


Sum-


Nand-

 


NOR-

 

XOR-

 

B. Floor plan of layout-

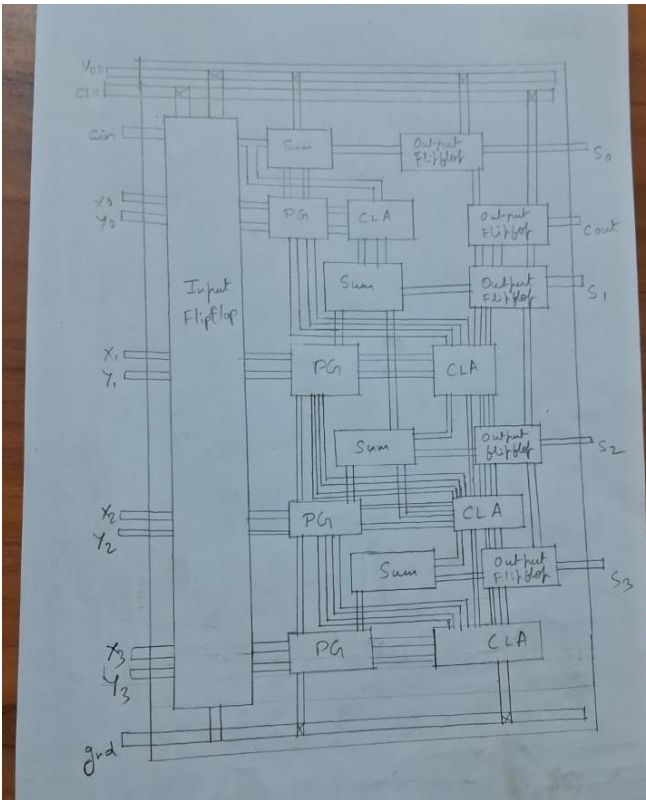

C. Horizontal and vertical pitches

```

Select topmost cell in the window
Root cell box:
width x height ( llx, lly ), ( urx, ury ) area (units^2)
microns: 97.92 x 115.56 ( -1.80, 34.83 ), ( 96.12, 150.39 ) 11315.64
lambda: 1088 x 1284 ( -20, 387 ), ( 1068, 1671 ) 1396992

```

D. Comparison-

Parameters	Pre-layout	Post-layout
CLA	2.296ns	2.26ns
D flip flop Tpcq	0.25ns	0.38ns
Full circuit	9.91×10^{-8}	$2.09 \times 10^{-7}s$
Hold time	0	$2 \times 10^{-21}s$

Maximum clock frequency- $1 / \text{minimum } T_{clk}$

Pre layout-

Maximum clock speed / freq = $1 / 2.7ns = 3.7 \times 10^8 \text{ Hz}$

Post layout-

Max clk freq = $1 / 2.8ns = 3.58 \times 10^8 \text{ Hz}$


XIII. VERILOG

We can observe the results from the gtk waveforms of the structural description of the circuit in verilog. When the inputs are available at the positive edge of the clock, the sum appears at the next positive edge which is visible below. Any change in the input now will be affecting the next clock.


```


kaadasika@Kaamya-laptop:~/iiith/2-1/vlsi/Project/V1$ v
kaadasika@Kaamya-laptop:~/iiith/2-1/vlsi/Project/V1$ v
VCD info: dumpfile 2023102034_gtkw.vcd opened for outp
clk=0 x=0000 y=0000 cin=0 C_out=x z=xxxx
clk=1 x=0000 y=0000 cin=0 C_out=x z=xxxx
clk=0 x=0000 y=0000 cin=1 C_out=x z=xxxx
clk=1 x=0000 y=0000 cin=1 C_out=0 z=0000
clk=0 x=0000 y=0001 cin=0 C_out=0 z=0000
clk=1 x=0000 y=0001 cin=0 C_out=0 z=0001
clk=0 x=0000 y=0001 cin=1 C_out=0 z=0001
clk=1 x=0000 y=0001 cin=1 C_out=0 z=0001
clk=0 x=0000 y=0010 cin=0 C_out=0 z=0010
clk=1 x=0000 y=0010 cin=0 C_out=0 z=0010
clk=0 x=0000 y=0010 cin=1 C_out=0 z=0010
clk=1 x=0000 y=0010 cin=1 C_out=0 z=0010
clk=0 x=0000 y=0011 cin=0 C_out=0 z=0011
clk=1 x=0000 y=0011 cin=0 C_out=0 z=0011
clk=0 x=0000 y=0011 cin=1 C_out=0 z=0011
clk=1 x=0000 y=0011 cin=1 C_out=0 z=0011
clk=0 x=0000 y=0100 cin=0 C_out=0 z=0100
clk=1 x=0000 y=0100 cin=0 C_out=0 z=0100
clk=0 x=0000 y=0100 cin=1 C_out=0 z=0100
clk=1 x=0000 y=0100 cin=1 C_out=0 z=0100
clk=0 x=0000 y=0101 cin=0 C_out=0 z=0101
clk=1 x=0000 y=0101 cin=0 C_out=0 z=0101
clk=0 x=0000 y=0101 cin=0 C_out=0 z=0101

```

 


Vivado-

 

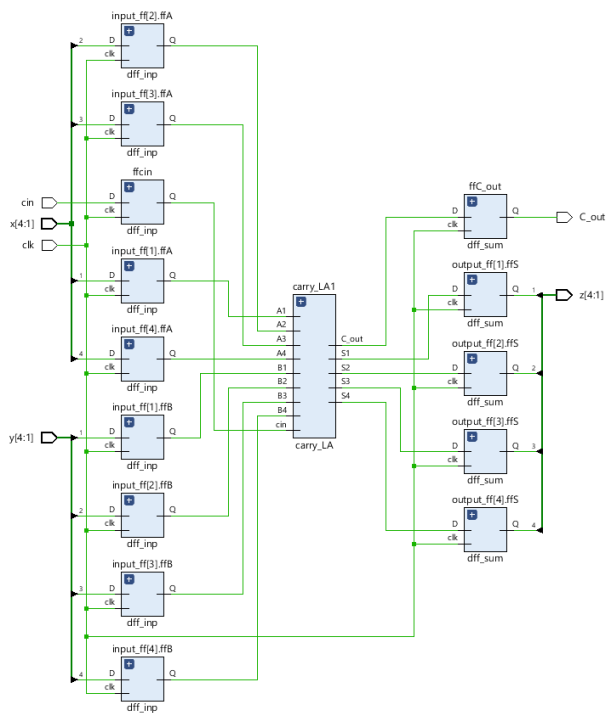


carry_LA1

 

XIV.FPGA

 The following drive link displays the working of FPGA and the oscilloscopes for the circuit. We use 3 oscilloscopes for 5 output bits. On giving an input combination, we observe the change in levels(VDD or GND) or the LED on FPGA for the next positive edge of clock.



<https://drive.google.com/drive/folders/18tlj9y4bYujJHjAKJuKM1SPlawF1IIGF?usp=sharing>

ACKNOWLEDGMENT

I thank the professor and the Tas for constant support throughout the project with claryfying doubts timely.

REFERENCES

- Carry Look-Ahead Adder - GeeksforGeeks
- A Proposed Design of Conventional 4-Bit Carry Look-Ahead Adder Improving Performance[1].pdf